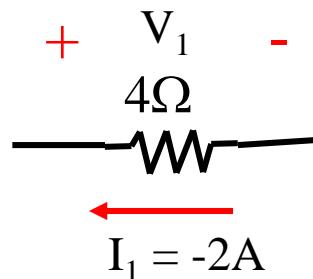


$$\mathbf{V}_1 = +\mathbf{I}_1 \mathbf{R}$$

$$\mathbf{V}_1 = +(2\text{A})(4\Omega)$$

$$\mathbf{V}_1 = +8\mathbf{v}$$



$$\mathbf{V}_1 = -\mathbf{I}_1 \mathbf{R}$$

$$\mathbf{V}_1 = -(-2\text{A})(4\Omega)$$

$$\mathbf{V}_1 = +8\mathbf{v}$$

$$\mathbf{V}_1 = +\mathbf{I}_1 \mathbf{R}$$

Kirchhoff's Current Law (**KCL**)


$$\sum I = 0 \quad \text{OR} \quad \sum I_{in} = \sum I_{out}$$

-- at any nodes
-- conservation of charge

Kirchhoff's Voltage Law (**KVL**)

$$\sum V = 0$$

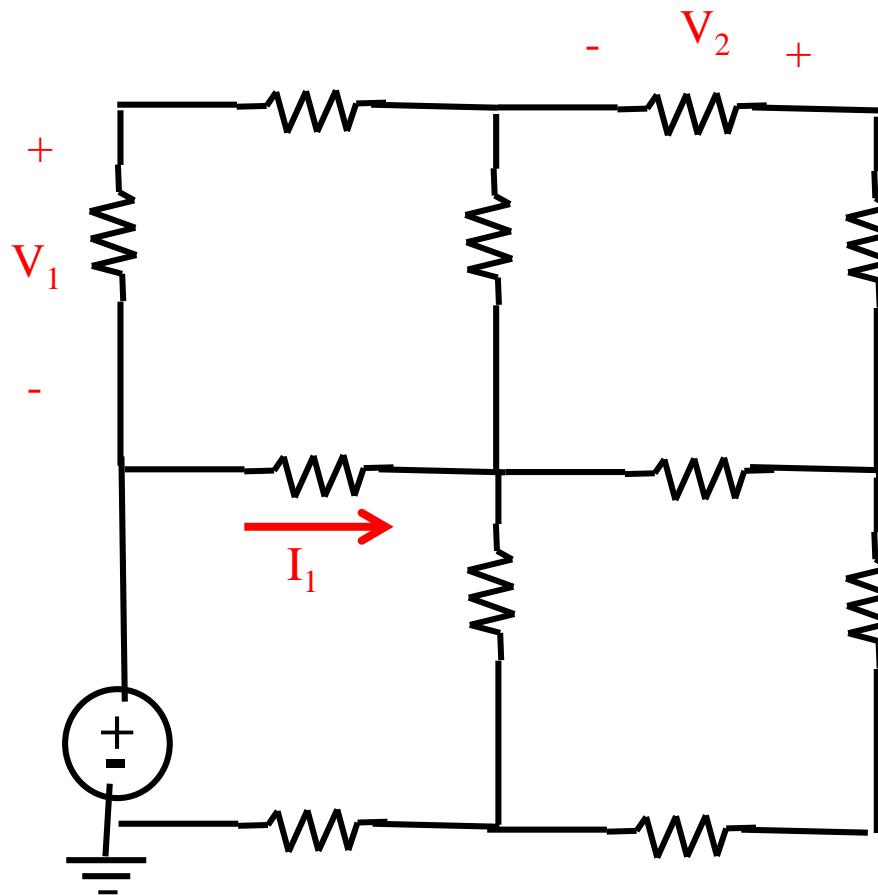-- at any closed loop
-- conservation of energy



$$V_1 = ?$$

$$V_2 = ?$$

$$I_1 = ?$$


$$V = IR$$

$$\sum I = 0$$

$$\sum V = 0$$

Nodal Analysis (using KCL)

$$\sum I = 0$$



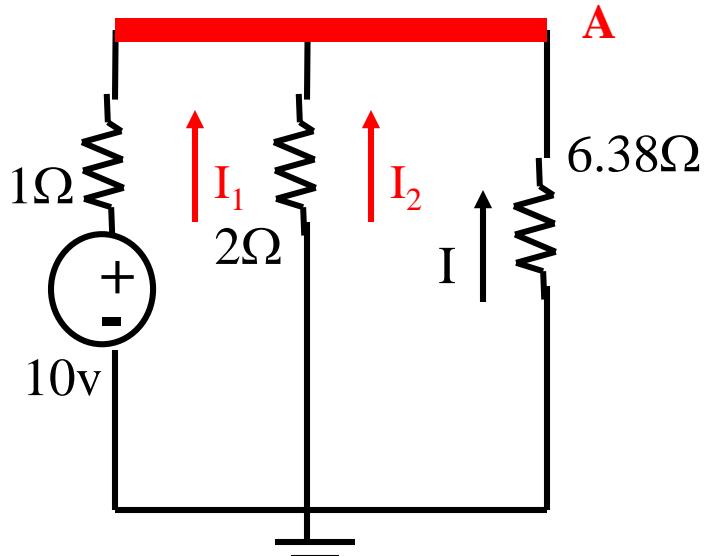


$$I_1 + I_2 + I = 0$$



$$\frac{(10 - V_A)}{1} + \frac{(0 - V_A)}{2} + \frac{(0 - V_A)}{6.38} = 0$$

$$V_A = 6.04v$$

$$I = -0.947A$$

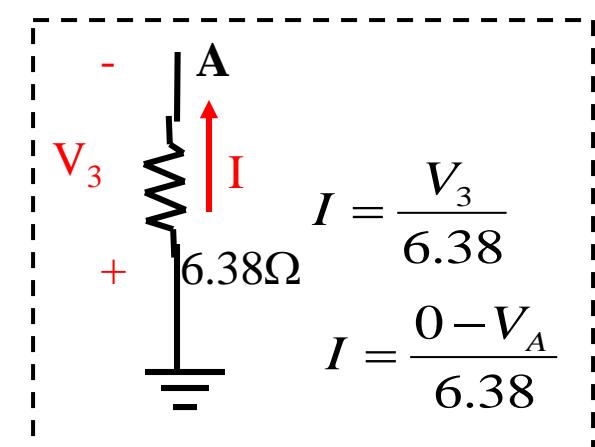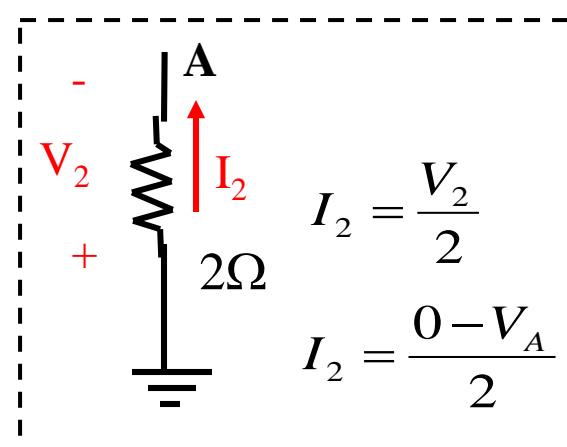
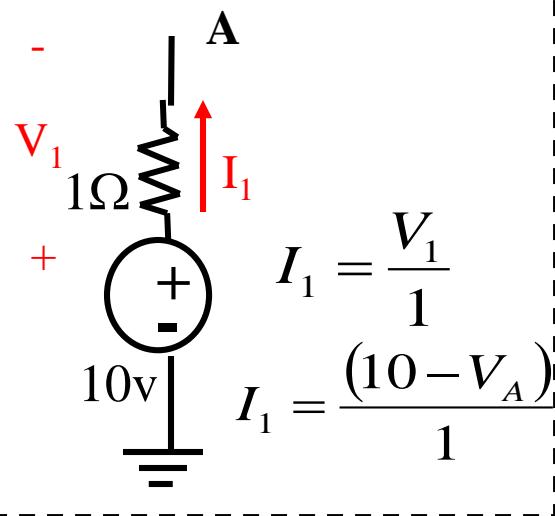


Superposition

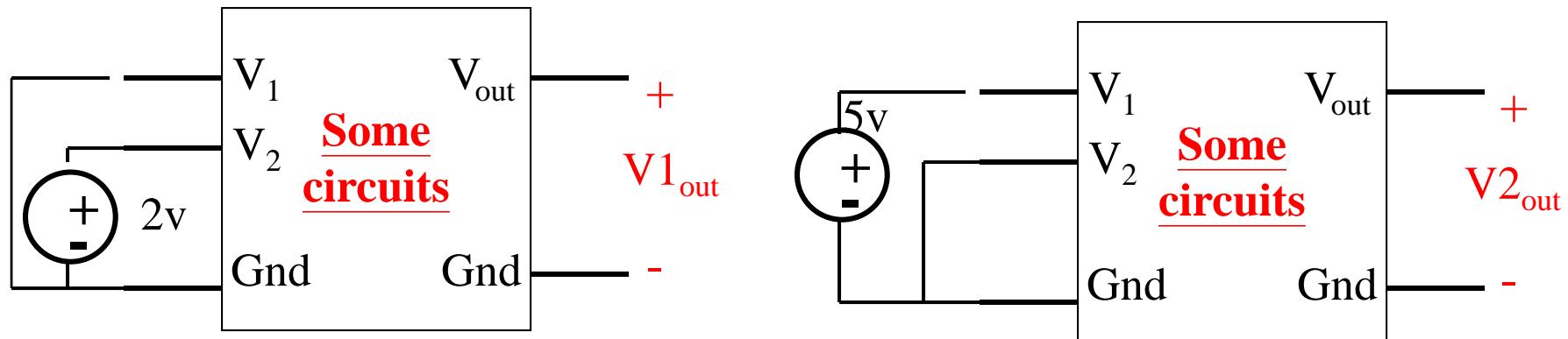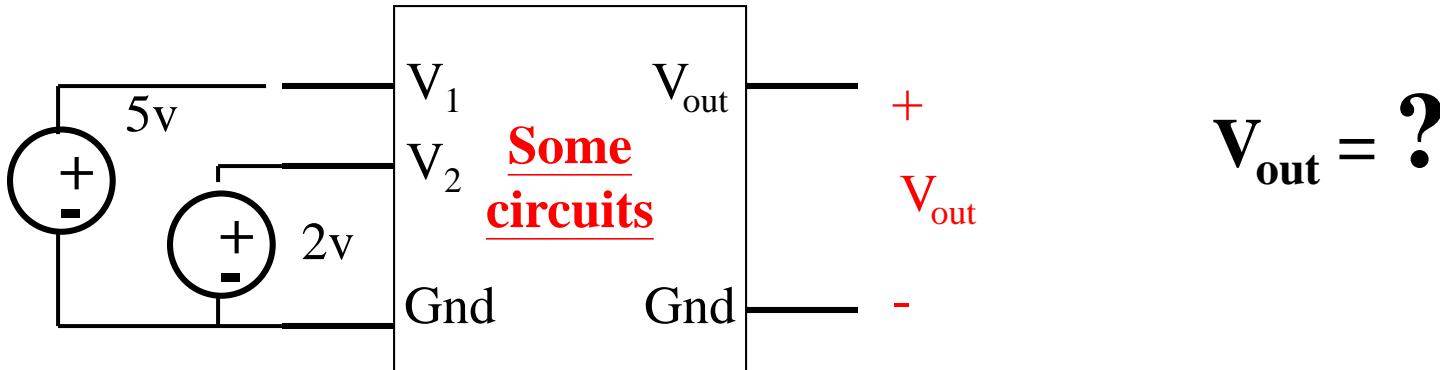


$$V_{out} = V_{1out} + V_{2out}$$

Superposition

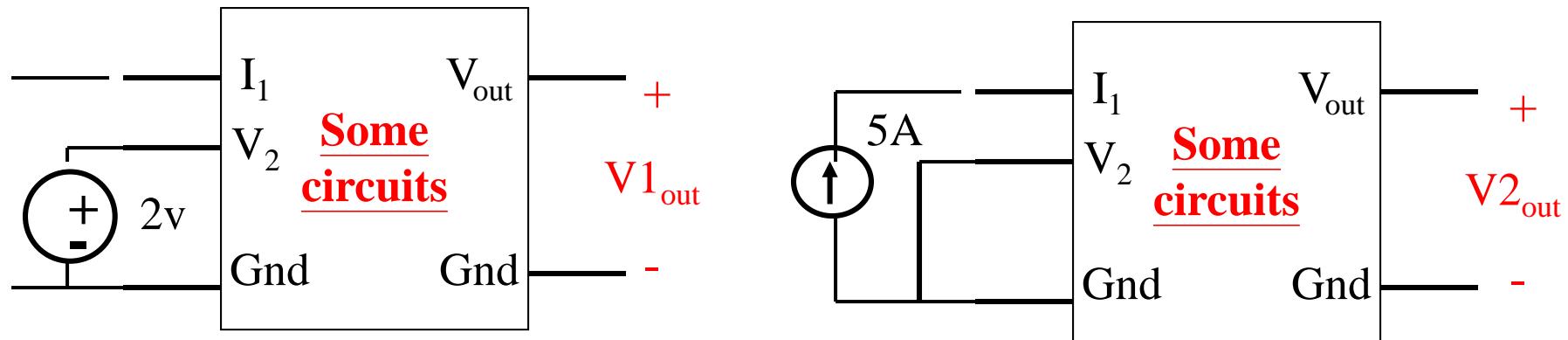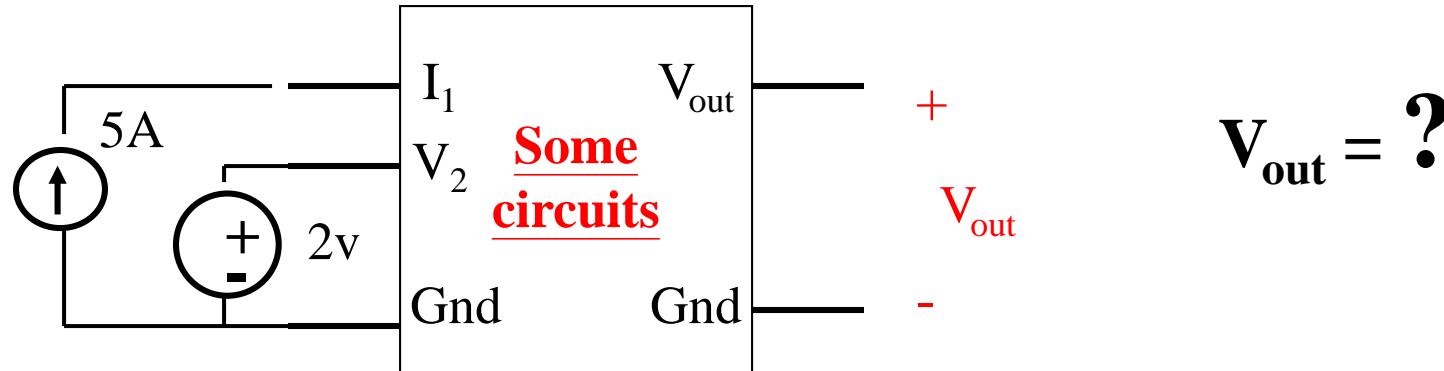

$$V_{out} = V_{1out} + V_{2out}$$


Superposition

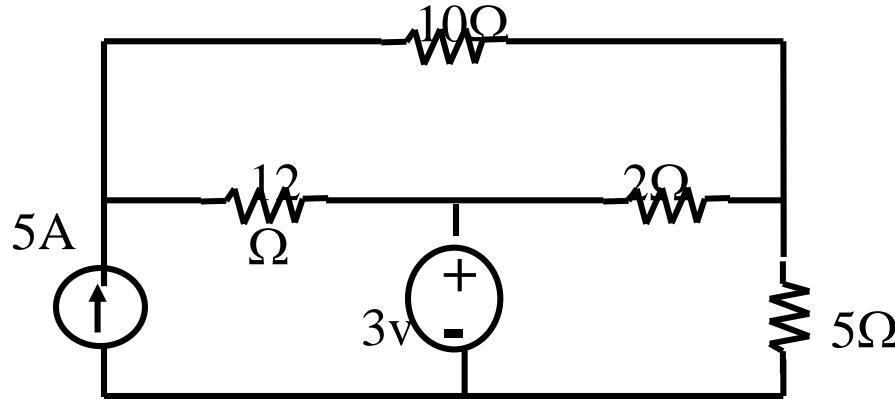


- **OPEN** the current source
- **SHORT** the voltage source

+
V_{out}
-

- **OPEN** the current source

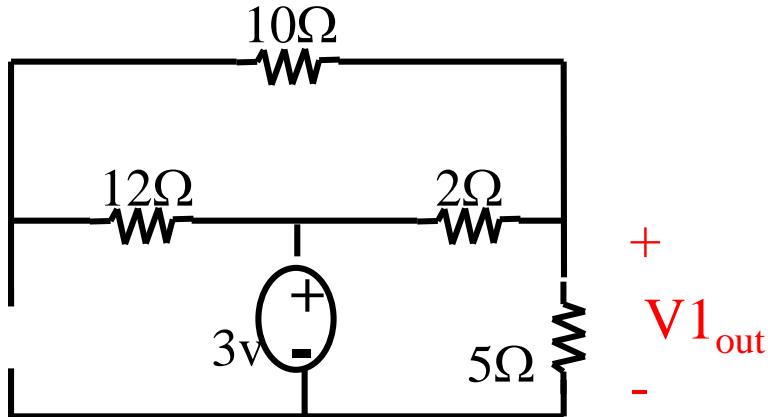

- **SHORT** the voltage source

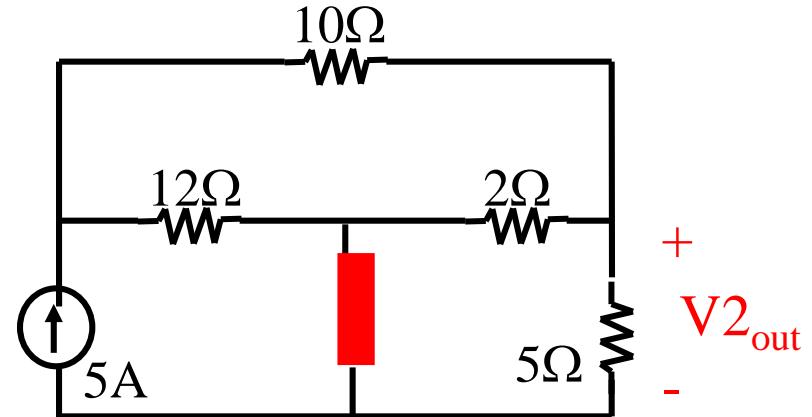

$$V_{\text{out}} = V1_{\text{out}} + V2_{\text{out}}$$

(Source Transform)

